

# PHYS 2321

## Week 6: Capacitance

### W6 Day 1 Outline

- 1) Hwk: Ch. 24 MiscQ. 1-13 odd Due Friday  
Prob. 1,5,6,7,10,11,13,16,21,22,24,38,39,40,53
- 2) Capacitors and capacitance
  - a. Examples of capacitors
  - b.  $C \equiv Q/\Delta V =$  charge per volt across capacitor
  - b.  $C = A\epsilon_0/d$  for parallel plate capacitor
- 3) Review Exam I (mean = 14.6/30)

Notes:

Try Practice Quiz for Ch. 24.

Watch YouTube video by Khan Academy

# Types of capacitors



By Eric Schrader from San Francisco, CA, United States - 12739s, CC BY-SA 2.0, <https://commons.wikimedia.org/w/index.php?curid=37625896>

# PHYS 2321

## Week6: Capacitance

### W6 Day 2 Outline

- 1) Hwk: Ch. 24 MiscQ. 1-13 odd Due Friday  
Prob. 1,5,6,7,10,11,13,16,21,22,24,38,39,40,53
- 2) Capacitors and capacitance
  - a.  $C \equiv Q/\Delta V$  = charge per volt across capacitor
  - b. Calculating capacitances
  - c.  $C = A\epsilon_0/d$  for parallel plate capacitor
  - d. Parallel and series connections

### Notes:

How Ch. 23 mean = 9.2/10 (checked P. 12,25, MQ 1,3,5)


Pick up Exam I after class (if you haven't already).

Try Practice Quiz for Ch. 24.

Watch YouTube video by Khan Academy
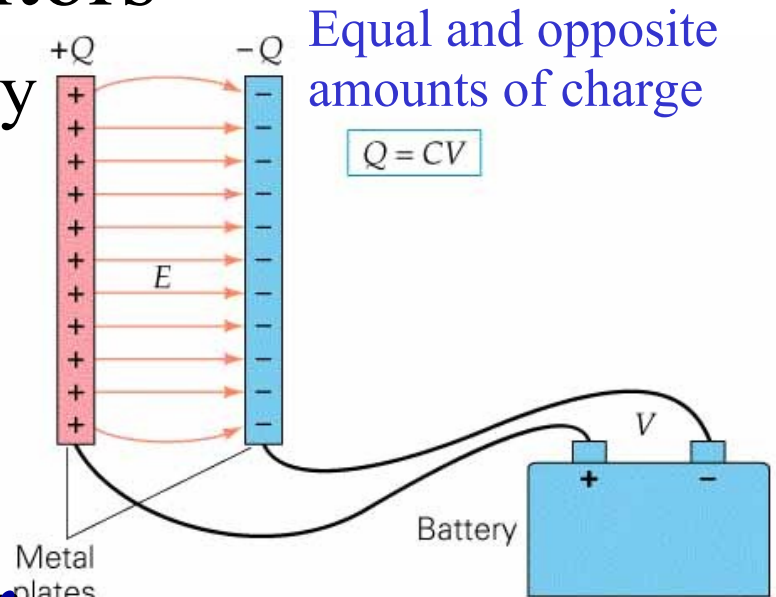
# Capacitors

- Charge separation stores energy
- Parallel Plates
  - Uniform E field
  - $V = \Delta V$  between plates



(a) Parallel-plate capacitor

- **Capacitance: the “charge per volt” on a capacitor**

$$C \equiv \frac{Q}{V}$$

Capacitance governs ...

How much charge is required to produce 1 volt “on” the capacitor ( $Q = CV$ ),

What the potential difference will be if  $\pm Q$  of charge is on the plates. ( $V = Q/C$ )

Units: 1 Farad = 1 Coulomb/Volt

# Compute Capacitance of P.Plate Capacitor

1) Determine E-field between plates.

$$E = \frac{\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} = \frac{\sigma}{\epsilon_0}$$

2) Find  $|\Delta V|$ .

$$|\Delta V| = Ed \equiv \frac{\sigma d}{\epsilon_0} = \frac{Qd}{A\epsilon_0}$$


3) Insert into  $C=Q/\Delta V$ , and

4) Eliminate Q:

$$C = \frac{QA\epsilon_0}{Qd} = \frac{A\epsilon_0}{d}$$

5) Add k for dielectric:

$$C = \kappa \frac{A\epsilon_0}{d}$$

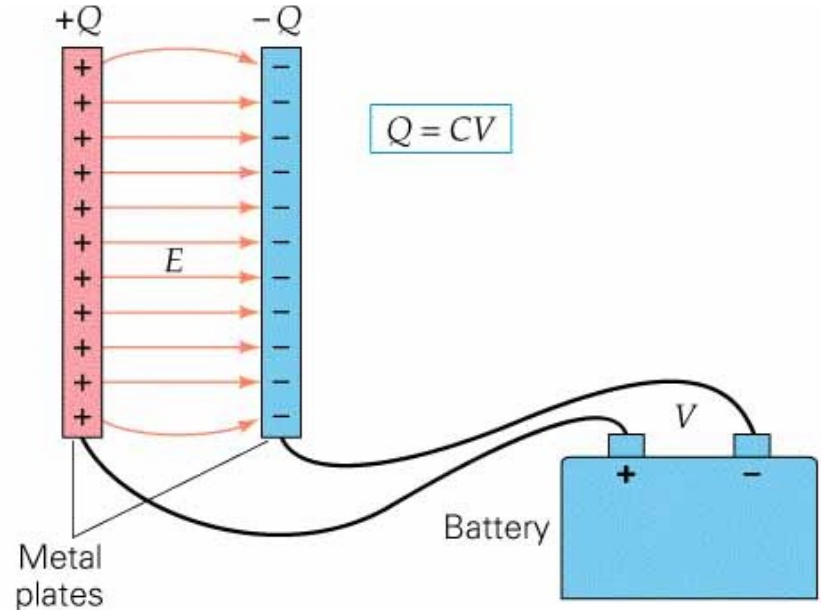

(a) Parallel-plate capacitor

For Parallel Plates only

$$\epsilon_0 = 8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2}$$

# Calculating Capacitance

1) Determine  $E$  inside capacitor. (May need Gauss's law.)

$$\Delta V = - \int_a^b \vec{E} \cdot d\vec{s}$$

2) Determine  $\Delta V$  between the plates.


3) Insert  $\Delta V$  into  $C = Q/\Delta V$ .

4) Cancel the  $Q$ 's.

5) Consider the dielectric filler. ( $C = \kappa C_0$ )

Example: concentric spheres

$$C_{spheres} = \frac{ab}{k_e(b-a)}$$

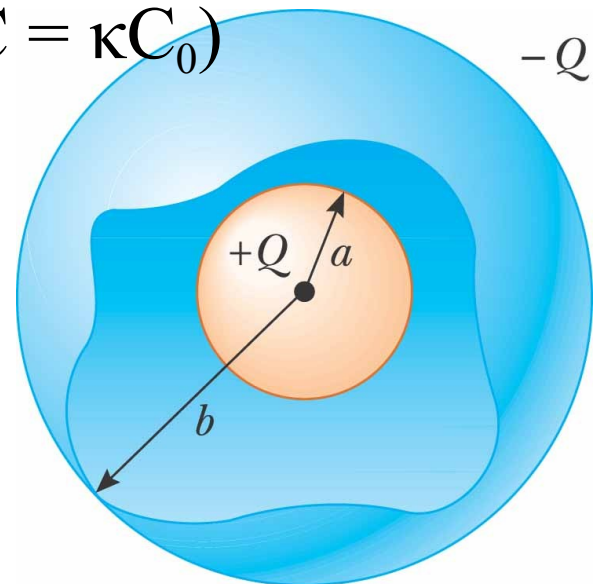

# Calculating Capacitance

Other examples:

1) Parallel plates

$$C = \frac{A\epsilon_0}{d}$$


2) Concentric cylinders

$$\frac{l}{2k_e \ln(b/a)} = \frac{2\pi l\epsilon_0}{\ln(b/a)}$$

3) Single sphere

$$C = 4\pi\epsilon_0 R$$

Example: concentric cylinders

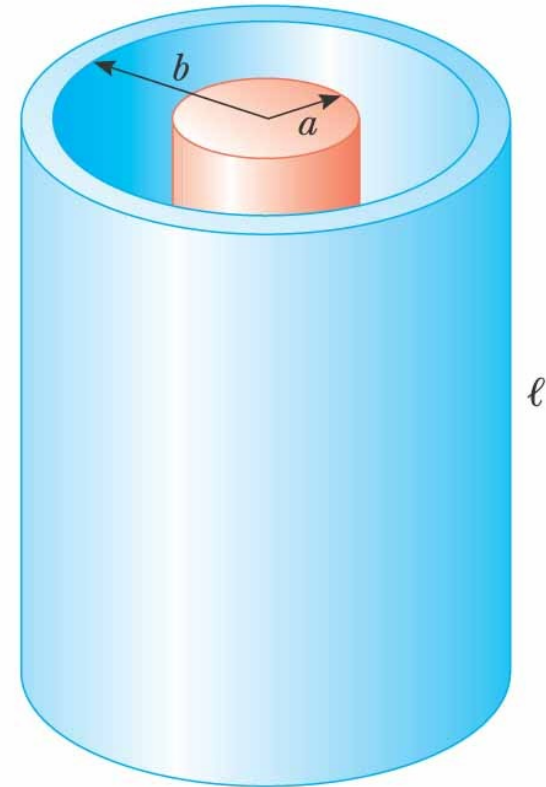


(a)

# Combining Capacitors

- Two fundamental arrangements: parallel and series.
- Characteristics of a parallel connection:

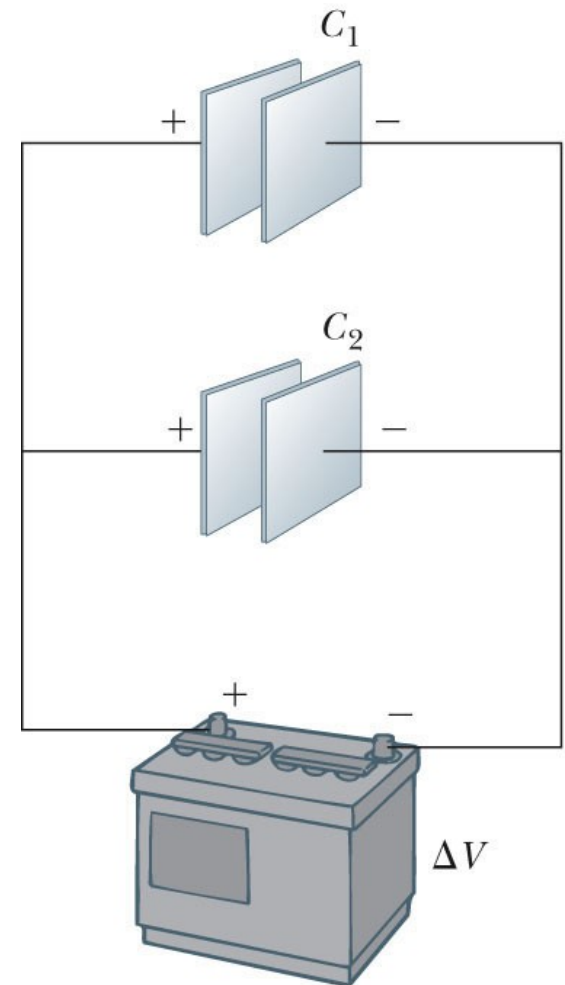- 1) The same  $\Delta V$  is across each capacitor.
- 2) If  $C_1 \neq C_2$ , then  $Q_1 \neq Q_2$ . (In general, the charges are unequal.)
- 3) Since the total area of the plates is greater for 2 capacitors than 1, the equivalent capacitance goes up.
- 4) For N capacitors in parallel:

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$



(a)




# Combining Capacitors

- Characteristics of a series connection:

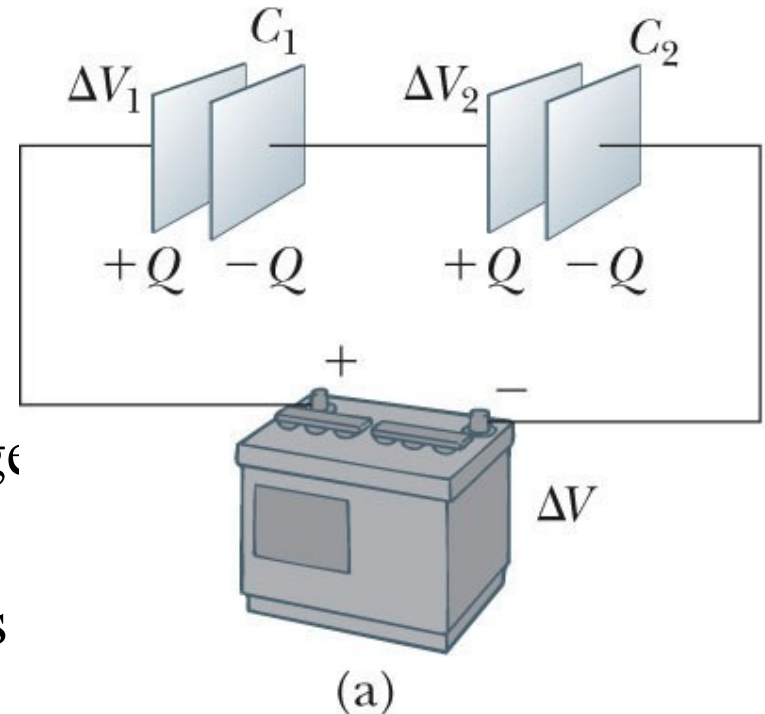- 1) The same charge  $Q$  exists on each plate!
- 2) If  $C_1 \neq C_2$ , then  $\Delta V_1 \neq \Delta V_2$ . (The voltage can be different on each cap..)
- 3) The sum of the  $\Delta V$ 's is the  $\Delta V$  across the battery.
- 4) The equivalent capacitance is less than even the smallest capacitor in series.
- 5) For  $N$  capacitors in series:


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$




© Thomson Higher Education
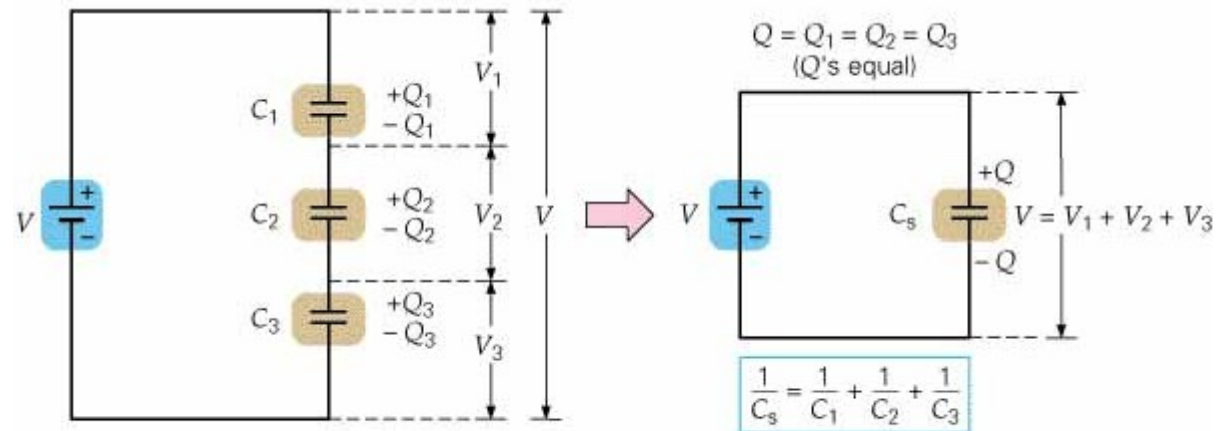
# Combining Capacitors

- Goal: combine them into one *equivalent capacitance*



(a) Capacitors in series

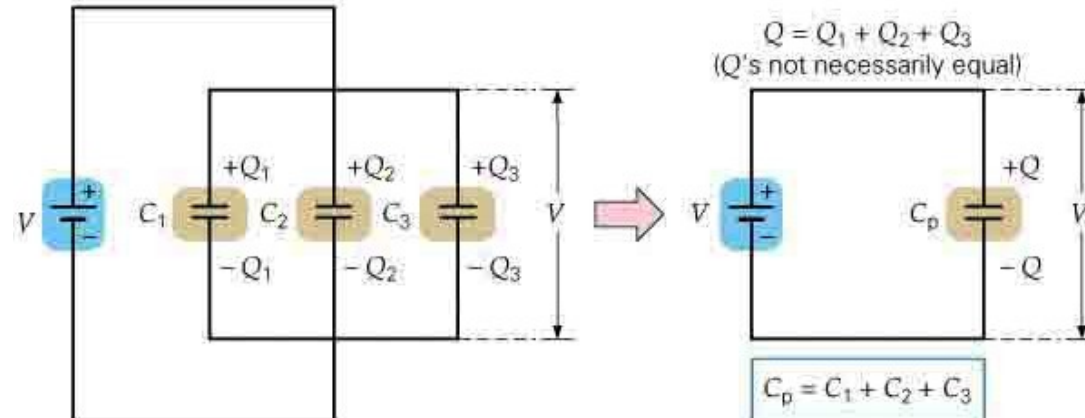


(b) Capacitors in parallel

# Capacitors in Series

Equivalent capacitor

- Charge in each plate is the same

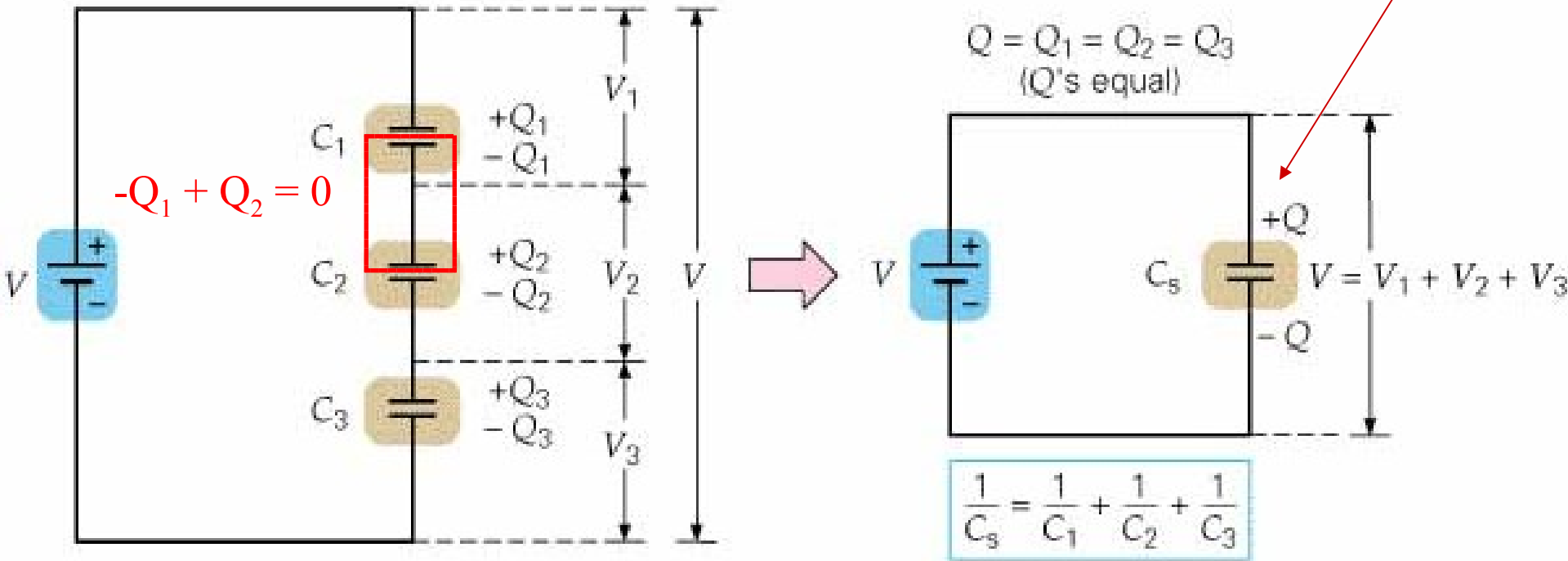

(a) Capacitors in series



$$C_1 = \frac{Q}{V_1}, C_2 = \frac{Q}{V_2}, C_3 = \frac{Q}{V_3}$$

$$V_1 = \frac{Q}{C_1}, V_2 = \frac{Q}{C_2}, V_3 = \frac{Q}{C_3}$$

$$V = V_1 + V_2 + V_3, V = \frac{Q}{C_s}$$
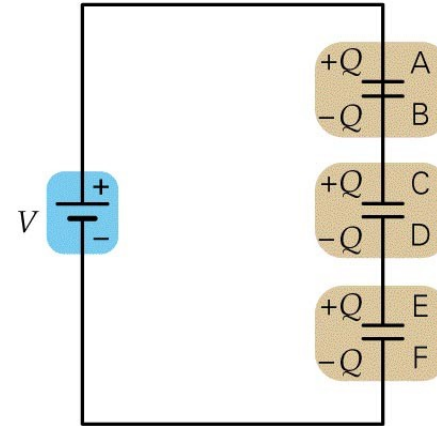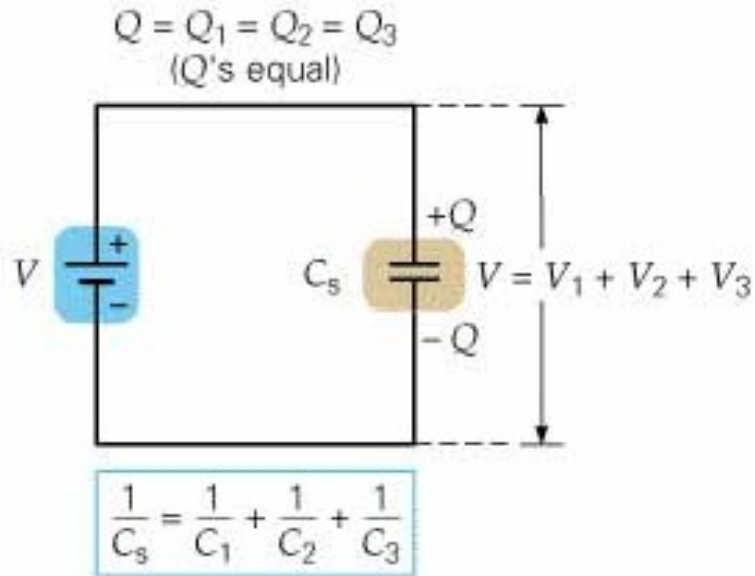
# Capacitors in Series

- Usually get  $C_s$  to get  $Q$ , then figure out the  $V$ 's




- Now expand the circuit back out

$$V_1 = \frac{Q}{C_1} \quad V_2 = \frac{Q}{C_2} \quad V_3 = \frac{Q}{C_3}$$

# Capacitors in Parallel

- Voltage on each plate is the same  $V = V_1 = V_2 = V_3$

Equivalent capacitor

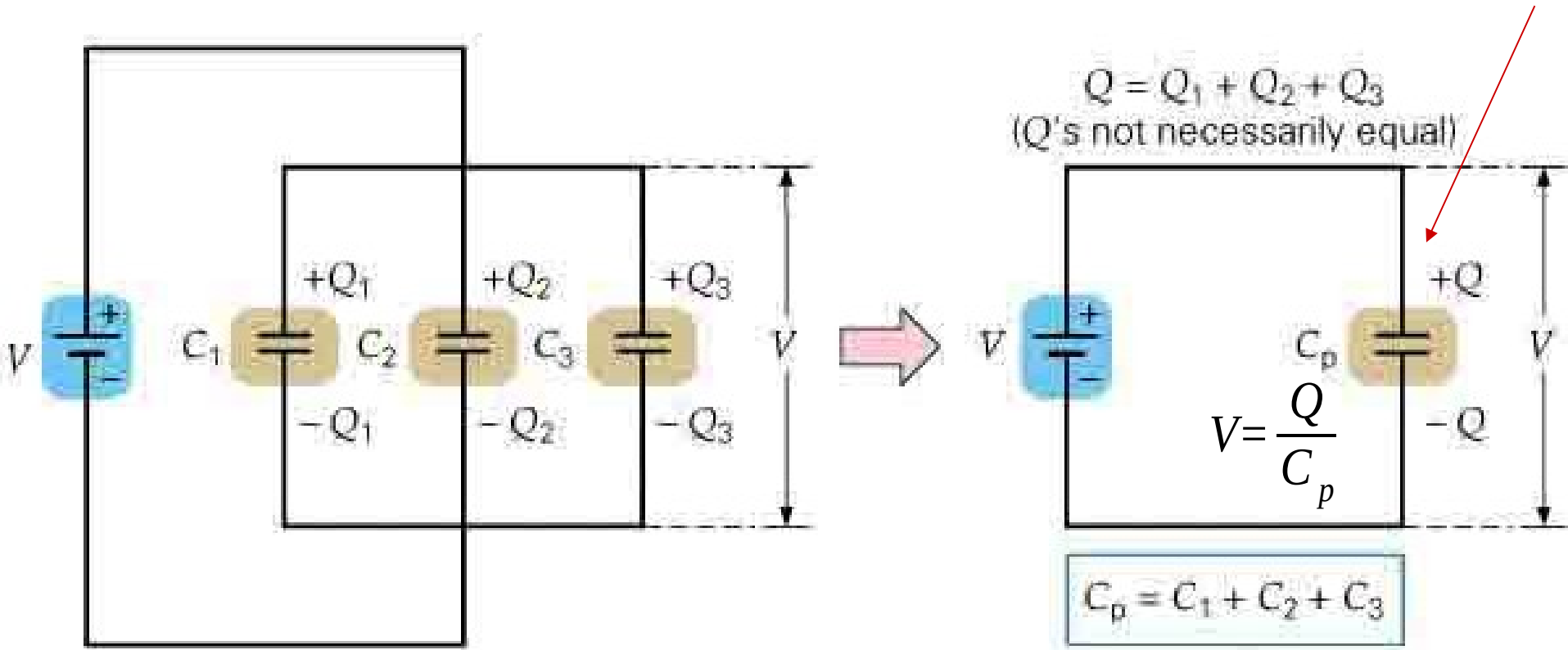


(b) Capacitors in parallel

$$Q = Q_1 + Q_2 + Q_3$$

$$Q_1 = C_1 V \quad Q_2 = C_2 V \quad Q_3 = C_3 V$$

# Combinations of Series and Parallel

- Get to one equivalent capacitor

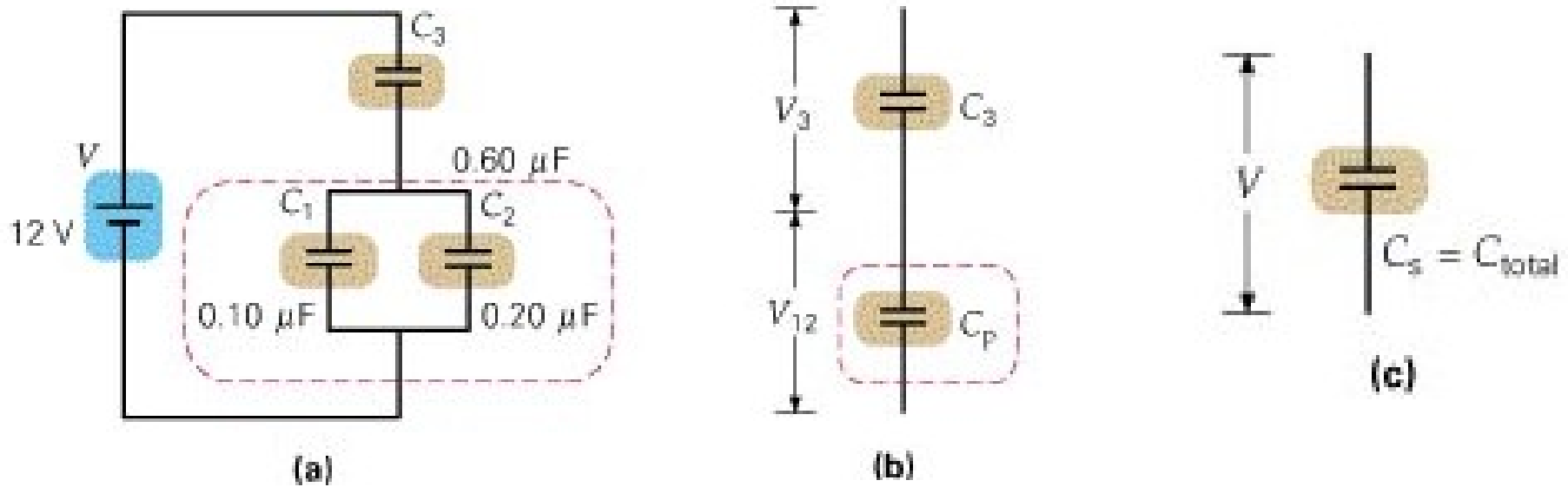

First combine  $C_1$  and  $C_2$  that are in parallel


Second combine  $C_{12}$  ( $C_p$  in diagram) and  $C_3$  in series

**CANNOT DO THE FOLLOWING:**

$C_3$  and  $C_1$  in series, then  $C_2$  in parallel or series

$C_3$  and  $C_2$  in series, then  $C_1$

# Equivalent Capacitance, Example

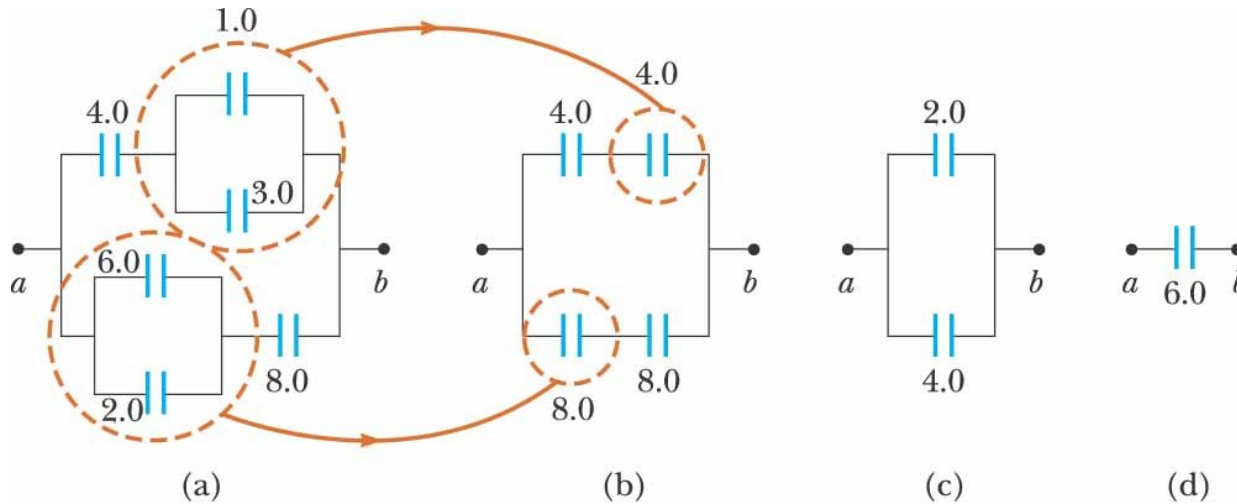

©2004 Thomson - Brooks/Cole


The 1.0- $\mu\text{F}$  and 3.0- $\mu\text{F}$  capacitors are in parallel as are the 6.0- $\mu\text{F}$  and 2.0- $\mu\text{F}$  capacitors

These parallel combinations are in series with the capacitors next to them

The series combinations are in parallel and the final equivalent capacitance can be found
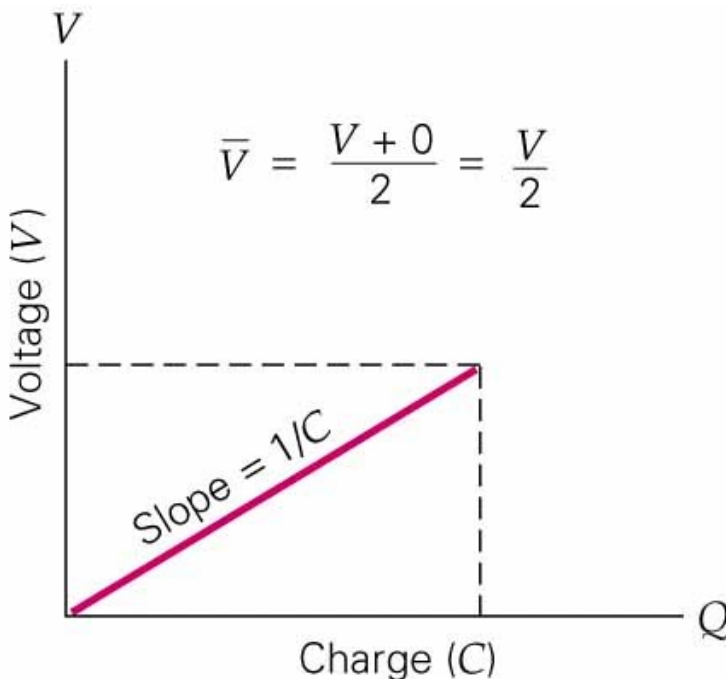
# Energy in a capacitor

- It takes energy to separate charge (& create E-field)
- The battery provides it, but that involves chemistry.
- Instead imagine charging plates “by hand”
  - Work by hand to move charge  $dq$ :  $dW = dq\Delta V = dqQ/C$
  - Total work to move all charge:



$$W = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$

OR ... area under V vs Q  
is energy!


$$U_c = \frac{1}{2} QV = \frac{Q^2}{2C} = \frac{1}{2} CV^2$$

**Energy of a charged capacitor**



# Dielectrics

- Capacitor charged and **battery disconnected**
  - $Q$  is constant - nowhere to go!

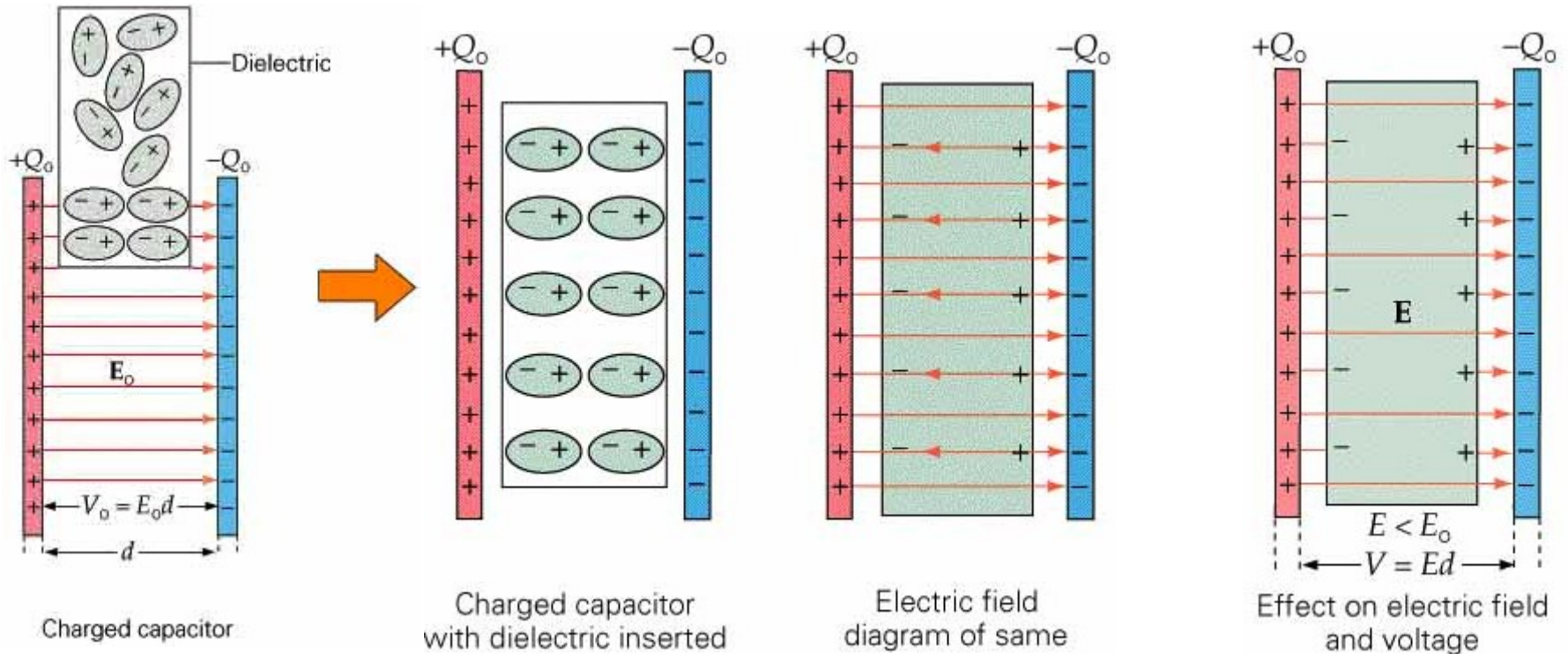


**TABLE 26.1****Approximate Dielectric Constants and Dielectric Strengths of Various Materials at Room Temperature**

<b>Material</b>	<b>Dielectric Constant <math>\kappa</math></b>	<b>Dielectric Strength<sup>a</sup> (<math>10^6</math> V/m)</b>
Air (dry)	1.000 59	3
Bakelite	4.9	24
Fused quartz	3.78	8
Mylar	3.2	7
Neoprene rubber	6.7	12
Nylon	3.4	14
Paper	3.7	16
Paraffin-impregnated paper	3.5	11
Polystyrene	2.56	24
Polyvinyl chloride	3.4	40
Porcelain	6	12
Pyrex glass	5.6	14
Silicone oil	2.5	15
Strontium titanate	233	8
Teflon	2.1	60
Vacuum	1.000 00	—
Water	80	—

<sup>a</sup> The dielectric strength equals the maximum electric field that can exist in a dielectric without electrical breakdown. These values depend strongly on the presence of impurities and flaws in the materials.
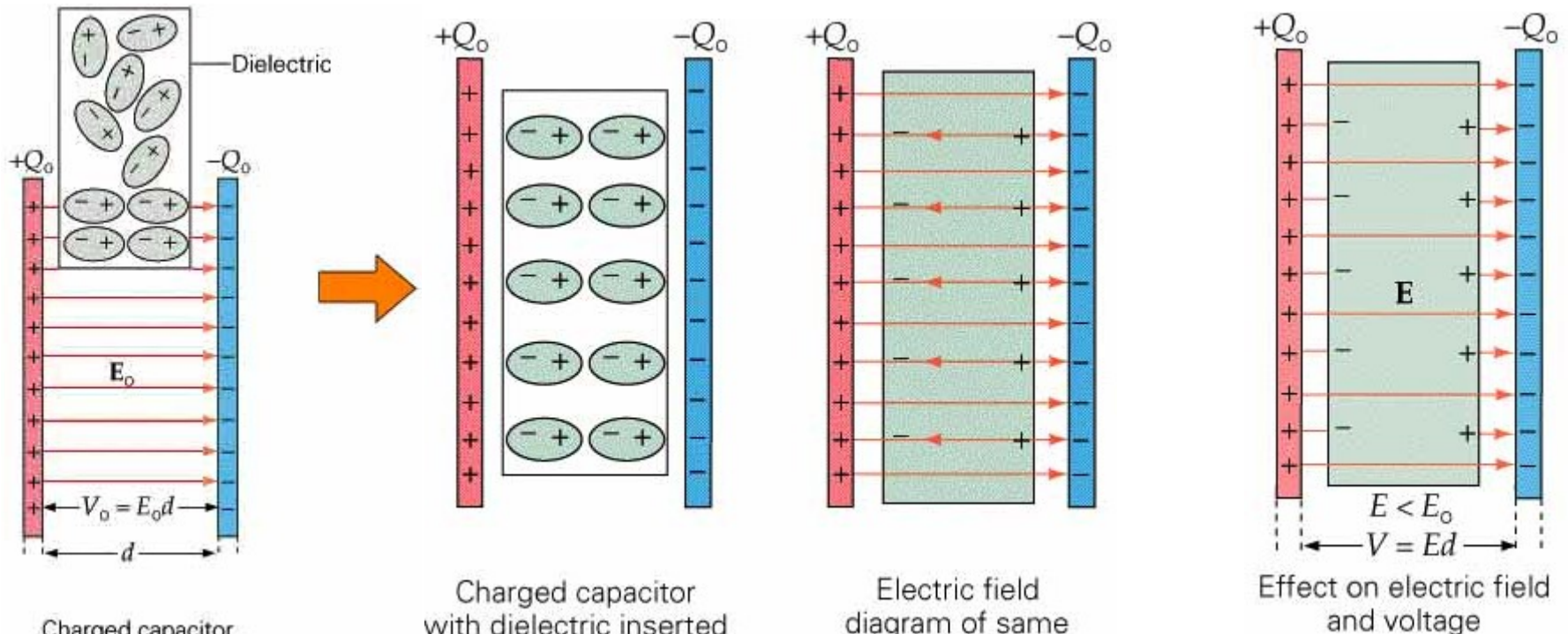
# Dielectrics

- Determine whether  $\kappa$  is greater than or less than 1:
  - 1) Molecules in dielectric get polarized
  - 2) Electric field between plates is reduced ( $Q$  is constant)
  - 3)  $\Delta V$  across plates is reduced (remember  $\Delta V = -Ed$ )
  - 4)  $U = 1/2 Q\Delta V$  is reduced, and so will be  $U = 1/2 Q^2/C$
  - 5)  $Q$  is constant, so  $C$  must have increased.
  - 6)  $C = \kappa C_0$  so  $\kappa > 1$



# Dielectrics

- Parallel Plates

$$C_o = \epsilon_o \frac{A}{d}$$

$$C = \epsilon \frac{A}{d} = K\epsilon_o \frac{A}{d}$$

Dielectric permittivity  $\epsilon = K\epsilon_o$

